

Combinational Logic



- All M-bit \rightarrow N-bit functions

Combinational Logic



- All M-bit \rightarrow N-bit functions
- But not all functions!
 - what if the input is not bounded? (e.g., large number addition)
 - what if the output is not bounded?


Combinational Logic



- All M-bit \rightarrow N-bit functions
- But not all functions!
 - what if the input is not bounded? (e.g., large number addition)
 - what if the output is not bounded?
- Multi-step Computation

Sequential Logic

 - Input – two sequences of bits.
- Output – a sequence of bits.



$$x_1 = [1, 0, 1, 0, 1, 1, 1, \dots]$$

$$x_2 = [0, 1, 1, 0, 1, 1, 0, \dots]$$

$$y = [1, 1, 0, 1, 0, 1, 0, \dots]$$

Adding two numbers from the last bit, remembering carry.

Sequential Logic


- Input – a sequence of M-bit units.
 - Output – a sequence of N-bit units.
- e.g., count the number of non-zero values in a sequence.

$$x = [0, 1, 0, 2, 3, \dots]$$

$$y = [0, 1, 1, 2, 3, \dots]$$

- Input – a sequence of M-bit units.
- Output – a sequence of N-bit units.
 - e.g., count the number of non-zero values in a sequence.
$$x = [0, 1, 0, 2, 3, \dots]$$
$$y = [0, 1, 1, 2, 3, \dots]$$
- Indexing notation
 - $x[t]$, $y[t]$, e.g., $x[1]=0$, $x[4]=2$, $y[3]=1$

 
- How to model time?
Can we change x at arbitrary time?



- this 1-bit signal changes whenever it likes.
- but we do not know if there are consecutive 0s!


Sequential Logic

- How to model time?


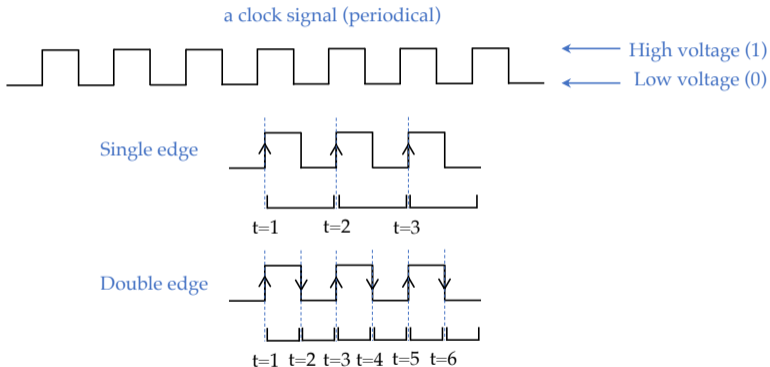


- There are devices for generating waves.

 - How to integrate clock into computation?




- Edge-trigger flipflops (ETFF)

  

- Set up I before clock tick.
- Hold I after clock tick.



- Edge-trigger flipflops (ETFF)

 

- Set up I before clock tick.
- Hold I after clock tick.
- O samples I at clock tick stage.


Sequential Logic

- Effective clock

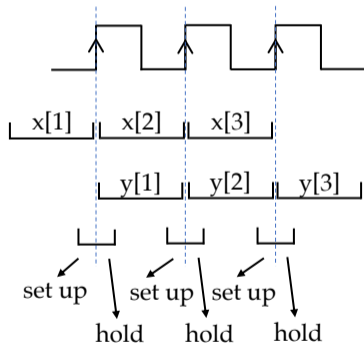 

Sequential Logic

- A **register** is a multi-bit ETFF

 

- It works together with the clock (CLK) to
 1. construct time sequence
 2. ensure output signal stability
- Requires input set up time and hold time.

- Build a sequential device.
count the number of non-zero values in a sequence

$$x = [0, 1, 0, 2, 3, \dots]$$
$$y = [0, 1, 1, 2, 3, \dots]$$


- Simplified for illustration.
 - Use only 1-bit output, which is equivalent to indicating whether the count is odd(1) or even(0).
 - Use 2-bit input

$$x = [0, 1, 0, 2, 3, \dots]$$
$$s = [0, 1, 1, 0, 1, \dots]$$

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

 

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0 0	0 1	0 1
0 1	0 1	1 0
1 0	0 1	1 0
1 1	0 1	1 0


$$\begin{aligned} s_{t+1} &= \bar{x}_1 \bar{x}_2 s_t + x_1 \bar{x}_2 \bar{s}_t + \bar{x}_1 x_2 \bar{s}_t + x_1 x_2 s_t \\ &= \bar{x}_1 \bar{x}_2 s_t + (x_1 + x_2) \bar{s}_t \\ &= \overline{(x_1 + x_2)} s_t + (x_1 + x_2) \bar{s}_t \\ &= (x_1 + x_2) XOR s_t \end{aligned}$$

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0
 
$$\begin{aligned} s_{t+1} &= \bar{x}_1 \bar{x}_2 s_t + x_1 \bar{x}_2 \bar{s}_t + \bar{x}_1 x_2 \bar{s}_t + x_1 x_2 s_t \\ &= \bar{x}_1 \bar{x}_2 s_t + (x_1 + x_2) \bar{s}_t \\ &= \overline{(x_1 + x_2)} s_t + (x_1 + x_2) \bar{s}_t \\ &= (x_1 + x_2) XOR s_t \end{aligned}$$




Sequential Logic

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0 0	0 1	0 1
0 1	0 1	1 0
1 0	0 1	1 0
1 1	0 1	1 0
 
$$\begin{aligned} s_{t+1} &= \overline{x_1} \overline{x_2} s_t + x_1 \overline{x_2} \overline{s_t} + \overline{x_1} x_2 \overline{s_t} + x_1 x_2 \overline{s_t} \\ &= \overline{x_1} \overline{x_2} s_t + (x_1 + x_2) \overline{s_t} \\ &= \overline{(x_1 + x_2)} s_t + (x_1 + x_2) \overline{s_t} \\ &= (x_1 + x_2) XOR s_t \end{aligned}$$



How to add clock?


Sequential Logic

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0 0	0 1	0 1
0 1	0 1	1 0
1 0	0 1	1 0
1 1	0 1	1 0
 
$$\begin{aligned} s_{t+1} &= \bar{x}_1 \bar{x}_2 s_t + x_1 \bar{x}_2 \bar{s}_t + \bar{x}_1 x_2 \bar{s}_t + x_1 x_2 s_t \\ &= \bar{x}_1 \bar{x}_2 s_t + (x_1 + x_2) \bar{s}_t \\ &= (\bar{x}_1 + x_2) s_t + (x_1 + x_2) \bar{s}_t \\ &= (x_1 + x_2) XOR s_t \end{aligned}$$




Sequential Logic

- Build a sequential device.

current input x_t \longrightarrow next count $s_{t+1} = x_t + s_t$
current count s_t

x_t	s_t	s_{t+1}
0	0	0
0	1	1
0	1	0
1	0	1
1	1	0
1	1	1
1	0	0
 
$$\begin{aligned} s_{t+1} &= \bar{x}_1 \bar{x}_2 s_t + x_1 \bar{x}_2 \bar{s}_t + \bar{x}_1 x_2 \bar{s}_t + x_1 x_2 s_t \\ &= \bar{x}_1 \bar{x}_2 s_t + (x_1 + x_2) \bar{s}_t \\ &= \overline{(x_1 + x_2)} s_t + (x_1 + x_2) \bar{s}_t \\ &= (x_1 + x_2) \text{ XOR } s_t \end{aligned}$$



- Build a second sequential device.

Infinite adder

$$1100101 + 1010010$$



reverse, bit by bit

$$x_1 = [1, 0, 1, 0, 0, 1, 1]$$

$$x_2 = [0, 1, 0, 0, 1, 0, 1]$$



$$y = [1, 1, 1, 0, 1, 1, 0, 1]$$

- Build a second sequential device.
 - how to indicate finishing?
 - add a valid signal

$$x_1 = [1, 0, 1, 0, 0, 1, 1, 0, 0, \dots]$$

$$x_2 = [0, 1, 0, 0, 1, 0, 1, 0, 0, \dots]$$

$$v_x = [1, 1, 1, 1, 1, 1, 1, 0, 0, \dots]$$



$$y = [1, 1, 1, 0, 1, 1, 0, 1, 0, 0, \dots]$$

$$v_y = [1, 1, 1, 1, 1, 1, 1, 1, 0, 0, \dots]$$

- Build a second sequential device.

Use 1-bit adder unit



- Build a second sequential device.

Use 1-bit adder unit



- $y[t + 1], CO[t + 1] = \text{Adder}(x_1[t], y_1[t], CI[t])$

- Build a second sequential device.

Use 1-bit adder unit




- $y[t + 1], CO[t + 1] = \text{Adder}(x_1[t], y_1[t], CI[t])$
- How to add clock?

Sequential Logic

- Build a second sequential device.


Add clock

 

Sequential Logic

- Build a second sequential device.

Add validation

 

$$x_1 = [1, 0, 1, 0, 0, 1, 1]$$

$$x_2 = [0, 1, 0, 0, 1, 0, 1]$$


$$v_x = [1, 1, 1, 1, 1, 1, 1, 0]$$

$$y = [1, 1, 1, 0, 1, 1, 0, \boxed{1}] \longrightarrow \text{one more carry!}$$

$$v_y = [1, 1, 1, 1, 1, 1, 1, 0]$$



Sequential Logic

Additional bit

 

Sequential Logic

Generalize the two systems

  

x — input
 y — output


$$y[t + 1], s[t + 1] = f(x[t + 1], s[t])$$

s — state

The feedback info.



Finite State Machine

 


- So initial state S_0


$$y_{t+1}, s_{t+1} = \text{FSM}(x_{t+1}, s_t)$$

- FSM(sequential logic) can compute more functions than combinational logic.
 - you can turn a sequence of M -bit inputs into one input, by concatenation.
 - thus FSM computes ∞ -bit to ∞ -bit functions, in theory.
- Does FSM compute all integer functions $y = f(x)$?
- **Computation theory** investigates this.


The conclusion

 

Turing Machine

 

Alan Turing (23 June 1912 – 7 June 1954)

 

- Three questions:
 1. Turing machine V.S. any machine
 2. Turing machine V.S. all integer functions
 3. Can we make them?

The Church-Turing Thesis



Alonzo Church
(June 14, 1903 – August 11, 1995)



Stephen Cole Kleene
(January 5, 1909 – January 25, 1994)

- It has been shown that Turing Machines have the same computation power as recursion(Kleene) and lambda calculus(Church), two other famous computation tools in the 1950s.
- It has been hypothesized that anything computable by a machine is computable by a Turing Machine.


Gödel Incompleteness



Kurt Gödel
April 28, 1906 – January 14, 1978

- It has been **proved** that there are integer functions that Turing machine cannot compute.

 - Turing machines fall back to FSM if the tape is finite!



- Wipes out the advantage of TM over FSM.

